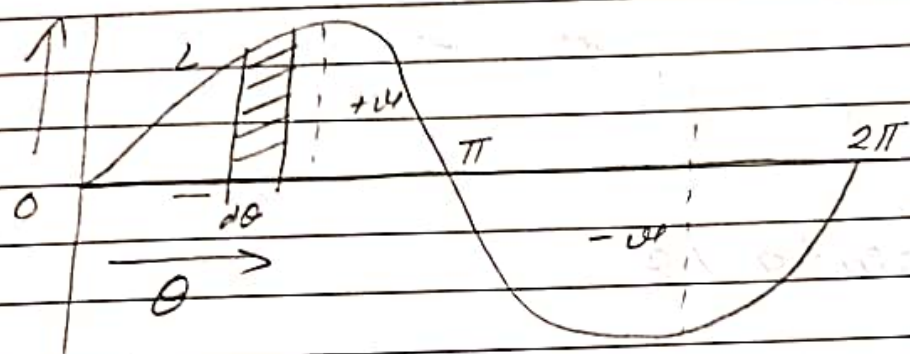


AC CircuitsAverage Value Sinusoidal

The alternating current varies sinusoidally as shown in fig 1



Area of element = $i d\theta$

$$(i) \quad i = I_m \sin \theta \quad \text{--- (1)}$$

Consider an elementary strip of thickness $d\theta$ in the +ve half cycle has been taken

Area of half cycle will be $(A) = \int_0^{\pi} i d\theta$

$$(A) = \int_0^{\pi} i \sin \theta d\theta$$

$$(A) = i_m \int_0^{\pi} \sin \theta d\theta \Rightarrow -i_m (-\cos(\pi) - \cos 0)$$

$$= i_m (1+1) \Rightarrow i_m (2) \Rightarrow 2I_m$$


Average value of current is

$$I_{av} = \frac{\text{Area of alternations}}{\text{base}}$$

$$I_{avg} = \frac{2I_m}{\pi}$$

$$I_{av} = \frac{2I_m}{3.14} = 0.537 I_m$$

RMS value of current:-

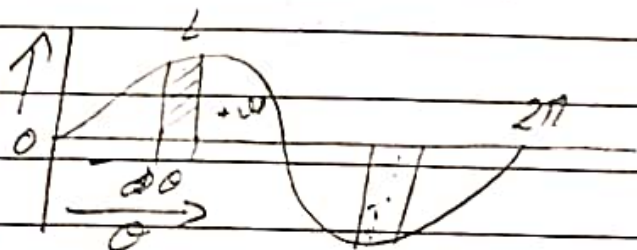

$$I_m^2 \int_0^{\pi} \sin^2 \theta d\theta$$

$$= I_m^2 \int_0^{\pi} \frac{1 - \cos 2\theta}{2} d\theta$$

$$= \frac{I_m^2}{2} \int_0^{\pi} (1 - \cos 2\theta) d\theta$$

~~$$= \frac{I_m^2}{2} \left[\theta - \left(\frac{\sin 2\theta}{2} \right) \right]_0^{\pi}$$~~

$$= \frac{I_m^2}{2} \left[\theta - 0 \right]_0^{\pi}$$

$$\cos 2\theta = 0$$

$$= \frac{I_m^2}{2} [\pi - 0]$$

$$= \frac{\pi I_m^2}{2} \Rightarrow \frac{3.14 \times I_m^2}{2}$$

$$I_{RMS} = \sqrt{\frac{\int \frac{I^2 I_m^2}{2} dt}{T}} \Rightarrow \frac{I_m}{\sqrt{2}} = 0.707 I_{mV} \text{ [max value]}$$

Form Factor:-

It is the ratio of R.M.S value to average value of alternating quantity is called form factor.

$$\frac{I_{RMS}}{I_{av}} = \frac{I_m/\sqrt{2}}{2I_m/\pi}$$

$$\frac{I_{RMS}}{I_{av}} = \frac{I_m}{\sqrt{2}} \times \frac{\pi}{2I_m}$$

$$\frac{I_{RMS}}{I_{av}} = \frac{\pi}{2\sqrt{2}}$$

$$\frac{I_{RMS}}{I_{av}} = \underline{\underline{1.11}}$$

Peak Factor:-

It is the ratio of maximum value to rms value of an alternating quantity is called peak factor.

$$P.f = \frac{I_m}{I_m/\sqrt{2}}$$

$$P.f = \frac{I_m}{I_m} \times \sqrt{2}$$


$$P.F = \sqrt{2}$$

$$\underline{\underline{P.F = 1.414}}$$

- Conductance
- Impedance
- ~~Admittance~~ Amperedence

⇒ AC circuit having resistance only:-

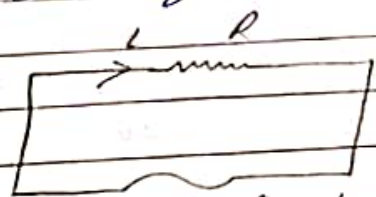Let an alternating voltage applied across the circuit is given by $V = V_m \sin \omega t$
The current can be defined by equation number (i)



$$V = V_m \sin \omega t \quad (i)$$

$$i = I_m \sin \omega t \quad (ii)$$


$$P = V i$$

$$= \frac{V_m I_m \sin^2 \omega t}{2}$$

$$= \frac{V_m I_m}{\sqrt{2} \sqrt{2}} (1 - \cos 2\omega t)$$

$$\frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} - \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos 2\omega t \quad \because \cos 2\omega t = 0$$

$$= \frac{V_m I_m}{\sqrt{2} \sqrt{2}}$$

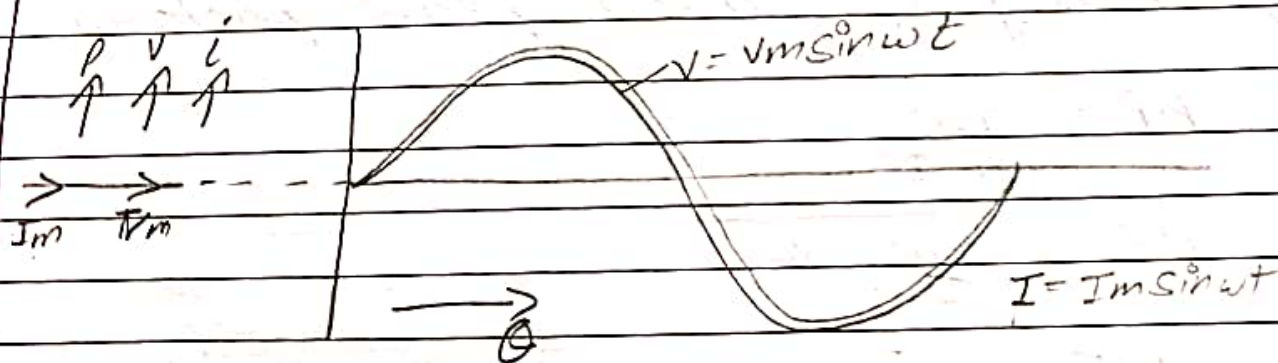


- In case of resistance there is no phase difference b/w voltage & current and the power obtained is maximum.

\Rightarrow AC circuit having inductor :-
 let the alternating voltage applied across a circuit is given by
 $V = V_m \sin \omega t$ — (I)
 As a result an alternating current I flows through the inductance which induces an EMF that is given by $e = -L \frac{di}{dt}$ — (II)

as per lenz's law this induced emf is equal and opposite to that of applied voltage from eq (II)
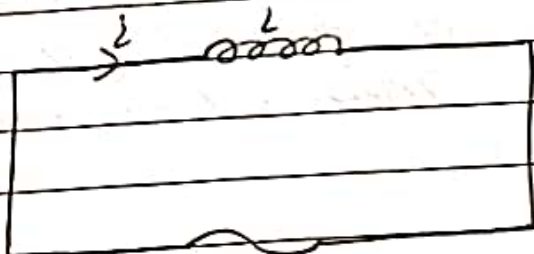
$$\begin{aligned}
 V &= -e \\
 V &= -(-L \frac{di}{dt}) \\
 V_m \sin \omega t &= L \frac{di}{dt}
 \end{aligned}$$



or

$$\int di = \int \frac{V_m \sin \omega t}{L} dt \text{ — (III)}$$

$$i = \frac{V_m}{\omega L} (-\cos \omega t)$$


$$i = \frac{V_m}{X_L} \left(\sin \omega t - \frac{\pi}{2} \right) \text{ — (IV)} \quad \therefore \frac{V_m}{X_L} = I_m$$

$$i = I_m \sin \left(\omega t - \frac{\pi}{2} \right) \text{ — (V)}$$


$$P = VI$$

$$\begin{aligned}
 P &= V_m \sin \omega t \times I_m \sin \left(\omega t - \frac{\pi}{2} \right) \\
 &= \frac{V_m I_m}{2} \times 2 \sin \omega t + \cos \omega t
 \end{aligned}$$
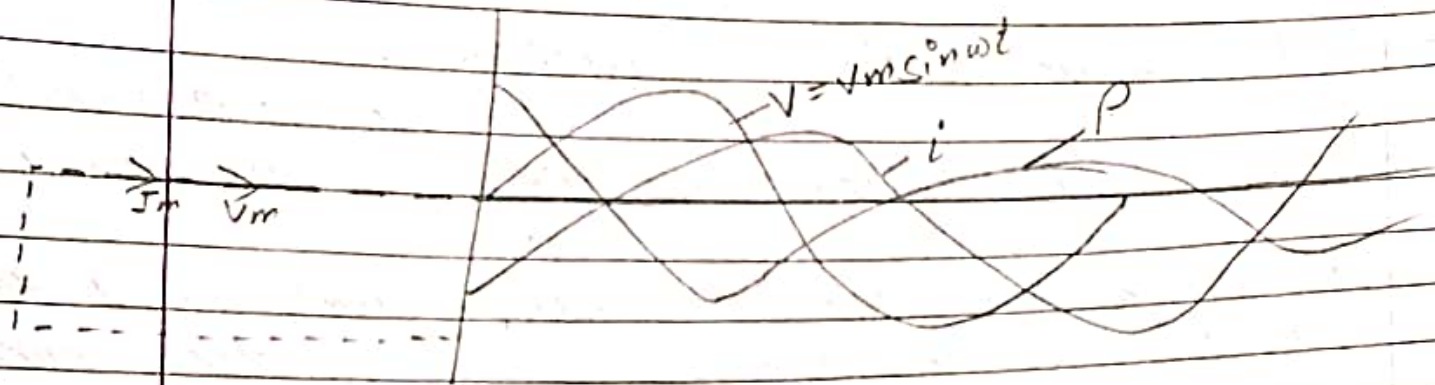
$$= \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \sin 2\omega t$$



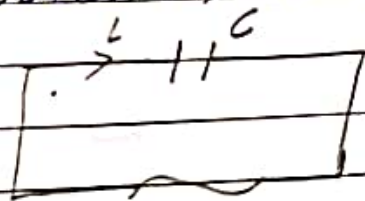⇒ AC circuit having ^{two capacitors} ~~1 conductor~~ only! -
 i.e. the alternating voltage applied across the circuit is given by same. charge on the capacitor is given by equation (i)
 Current flowing to the circuit $i = \frac{dq}{dt}$



$$V = V_m \sin \omega t \quad \text{--- (i)}$$


$$q = CV \quad \text{--- (ii)}$$

$$i = \frac{dq}{dt} \quad \text{--- (iii)}$$

$$i = \frac{d(CV)}{dt} \Rightarrow dC \frac{V_m \sin \omega t}{dt}$$

$$i = \omega C V_m \cos \omega t = \frac{V_m \sin(\omega t + \frac{\pi}{2})}{1/\omega C}$$
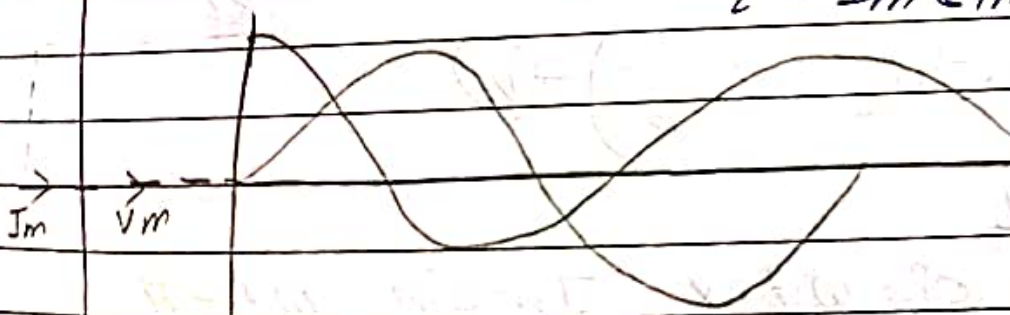
$$i = I_m \sin(\omega t + \frac{\pi}{2}) \quad \text{--- (vi)}$$



Numerical :-

Ques. An AC circuit consist of a pure resistance of 10 ohm and is connected across a supply of 230 V , 50 Hz . Calculate :- (1) the current, (2) power consumed and (3) expression, (4) voltage and current.

$$V = IR$$

$$\frac{V}{R} = I \Rightarrow I = \frac{230}{10} \Rightarrow \underline{\underline{23 \text{ A}}}$$

$$(i) I = 23 \text{ A}$$

$$(ii) P = VI$$

$$P = 230 \times 23$$

$$P = 529 \text{ W}$$

$$(iii) V_m = \sqrt{2} V$$

$$= 1.41 \times 230 = 325.2 \text{ V}$$

$$(iv) \omega = 2\pi f$$

$$= 2 \times 3.14 \times 50 = 314$$

$$(v) V = V_m \sin \omega t$$

$$= 325.2 \sin(314)$$

$$= -0.7 \times 325.2$$

$$= -233.9$$

Quest- An inductive coil having negligible resistance
0.1 Henry inductance is connected across
200V, 60 Hz supply. find

- a.) Inductive Reactance
- b.) RMS value of current
- c.) Power
- d.) Expression for voltage and current

$$L = 0.1 \text{ H}$$

$$V = 200 \text{ V}$$

$$f = 60 \text{ Hz}$$

(a)

$$X_L = \omega L$$

$$= 2\pi f L$$


$$= 2\pi \times 60 \times 0.1 = 37.68 \Omega$$

$$X_L = 37.68 \Omega$$

(b)


$$I_{\text{rms}} = \frac{V_{\text{rms}}}{X_L} = \frac{200}{37.68} = 5.31$$

RLC series circuit :-

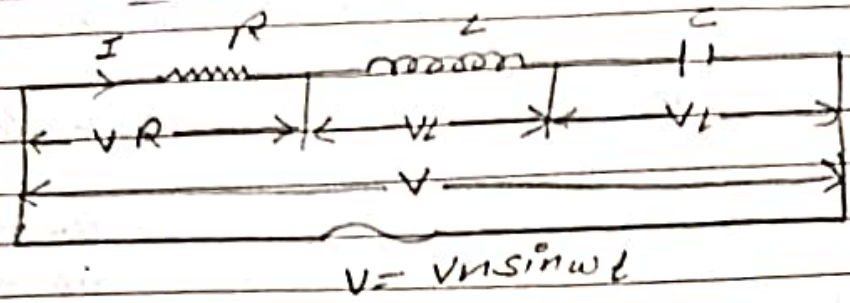

$$\begin{aligned} V_R &= IR \\ V_L &\Rightarrow I X_L \\ V_C &\Rightarrow I X_C \end{aligned}$$

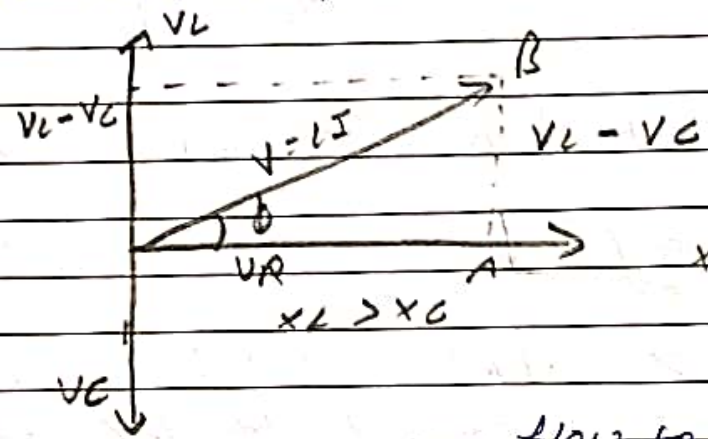A circuit which have a pure resistance of $R \Omega$, a pure inductance of L Henry and a pure capacitor of capacitance and cone are connected in series is known as RLC series circuit.



$$\begin{aligned} V_L &= \omega L \cdot 0.07 + L \\ X_C &= \frac{1}{\omega C} = \frac{1}{2\pi f C} \end{aligned}$$

When a resulting current ~~flow to the~~ ^{flow to the} circuit the voltage across each component will be.

The phaser diagram is show in Fig = 2 their current is taken as the reference pho since voltage across inductance V_L leads the current I by 90° and voltage across capacitance V_C lags the current by 90° .

If V_L is greater then V_C the circuit behave as an inductive circuit but when V_L is less then V_C the ^{inductive} circuit behave as a capacitive

Circuit. From the phaser diagram the circuit is consider for the inductive circuit.

$$V = \sqrt{(V_R)^2 + (V_L - V_C)^2} \quad \leftarrow \text{from phaser diagram.}$$

$$V = \sqrt{(IR)^2 + (IX_L - IX_C)^2}$$

$$V = \sqrt{I^2 (R^2 + (X_L - X_C)^2)}$$

$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$

$$V_R = IR \quad \text{--- (i)}$$

$$V_L = IX_L \quad \text{--- (ii)}$$

$$V_C = IX_C \quad \text{--- (iii)}$$

$$X_L = \omega L = 2\pi fL$$

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi fC}$$

$$X \left[V = I \sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC} \right)^2} \right]$$

$$V = I \sqrt{R^2 + (X_L - X_C)^2}$$

$$V = IZ$$

Where $Z = \sqrt{R^2 + (X_L - X_C)^2}$ it is the total opposition offered to the flow of alternating current by an RLC ~~circuit~~ ^{series} circuit and it known as impedance of the circuit.

Formula:- $\phi = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right)$

⇒ Three Cases of RLC series circuit

1) When X_L is greater than X_C the phase angle is +ve. In this case the

circuit current leads behind the applied voltage and power factor is leading the equation for the current will be $I = I_m \sin(\omega t - \phi)$

2) When X_L is less than X_C angle is $-ve$ in this case circuit behaves as an RC series circuit. The circuit current leads the applied voltage and power factor is leading and in this case the equation of current is $I = I_m \sin(\omega t + \phi)$
 $\phi = \pi/2$

3) When X_L is equal to X_C the phase angle is zero and the circuit behaves as a pure resistive circuit in this case the circuit current is in phase with the applied voltage and the equation of current will be $I = I_m \sin \omega t - R$

current change every time in each case.


⇒ Series Resonance:- In an RLC series circuit when circuit current is in phase with the applied voltage the circuit is said to be series resonance and $X_L = X_C$
 $Z = \sqrt{R^2 + (X_C - X_L)^2}$
 $Z_H = \sqrt{R^2} \Rightarrow Z_H = R$
 $(I_H = V/Z_H)$

⇒ Resonance frequency:- The value of x_L and x_C can be change by changing this applied ~~sub~~ supply frequency. So that the series resonance frequency will be

$$x_L = x_C$$

$$2\pi f R L = \frac{1}{2\pi f R C}$$

$$(2\pi f R L) 2\pi f R C = 1$$

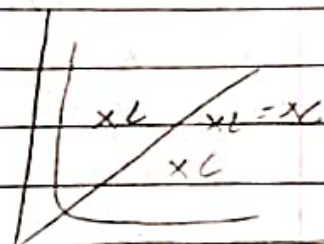

$$4\pi^2 f^2 R^2 L C = 1$$



$$f^2 R^2 L C = \frac{1}{4\pi^2}$$

$$f^2 = \frac{1}{4\pi^2 R^2 L C}$$

$$f = \frac{1}{2\pi R \sqrt{L C}}$$

$$f = \frac{1}{2\pi \sqrt{L C}}$$

⇒ Resonance Curve:-

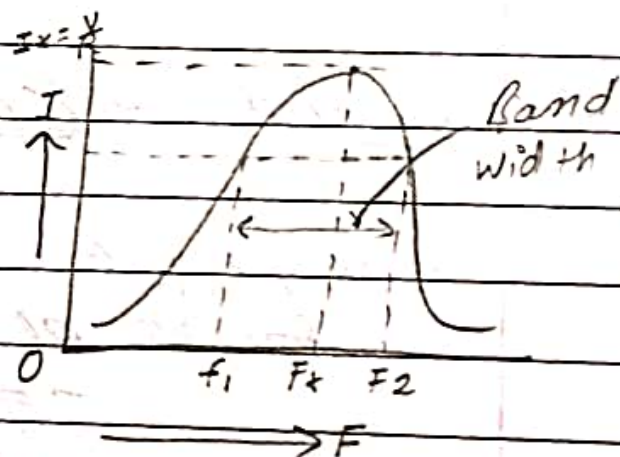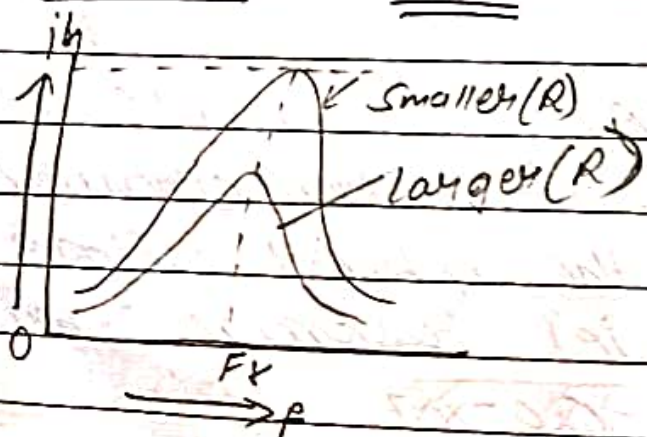

Quality factor or Q factor:-

The factor by which the potential difference across L or C exceeds to that of applied voltage is called Q factor of the series resonant circuit.

$$Q \text{ factor} \Rightarrow \frac{I_R \times L}{I_R R} = \frac{\omega L}{R}$$

$$= 2\pi f L \frac{1}{R}$$


$$= \frac{1}{2\pi f R C} \quad \because f = \frac{1}{2\pi \sqrt{LC}}$$

$$= 2\pi \times \frac{1}{2\pi R \sqrt{LC}}$$


$$= \frac{1}{R \sqrt{LC}}$$

Parallel resonance:-

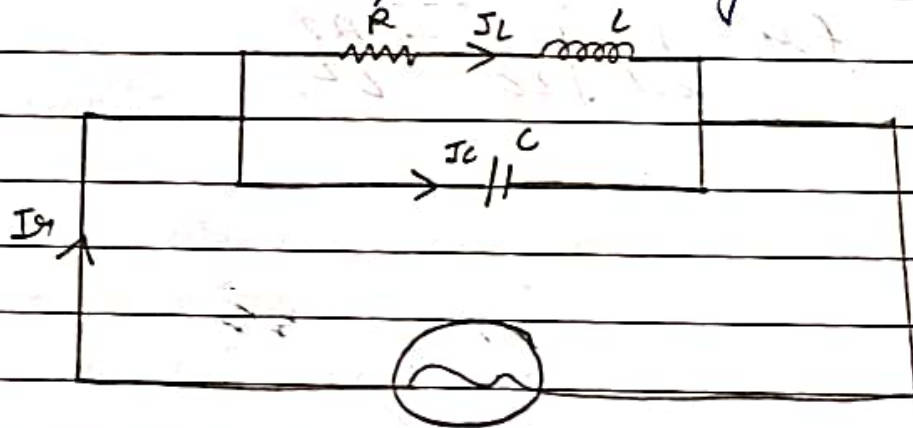An AC circuit having an inductor & capacitor in parallel is set to be parallel resonance when the circuit current is in phase with the applied voltage.



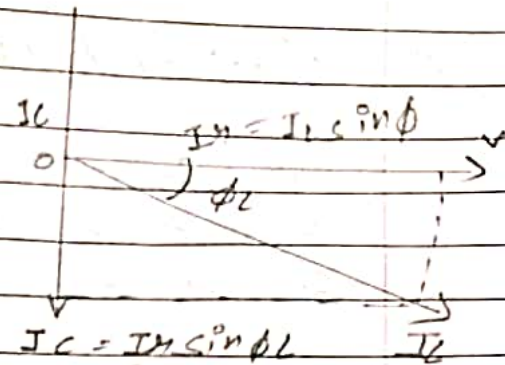The circuit current I_R will be in phase with the supply voltage when
 $I_C = I_L \sin \phi$



$$V = I_C X_C$$

$$V = I_L Z_L$$

$$\sin \phi_L = \frac{X_L}{Z_L}$$

$$\frac{V}{X_C} = \frac{V}{Z_L} \times \frac{X_L}{Z_L}$$

OR

$$X_L X_C = Z_L^2$$

$$\frac{\omega L}{\omega C} = Z_L^2 = (R^2 + X_L^2)$$

$$\frac{L}{C} = R^2 + (2\pi f H L)^2$$

$$2\pi f H L = \sqrt{\frac{L}{C} - R^2}$$

$$f H = \frac{1}{2\pi L} \sqrt{\frac{L}{C} - R^2}$$

$$f H = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

→ Comparison of Series & Parallel Resonance Circuits :-

Sr. no	Particulars	Series circuit	Parallel circuit
1	Impedance	Minimum i.e. $Z_R = R$	Maximum i.e. $Z_R = \frac{1}{CR}$
2	Current	Maximum i.e. $I_R = V/R$	Minimum i.e. $I_R = V/Z_R$
3	Resonant frequency (f_R)	$f_R = \frac{1}{2\pi\sqrt{LC}}$	$f_R = \frac{1}{2\pi\sqrt{\frac{1}{LC} - R^2}}$
4	Power factor (P.f)	unity	unity
5	Q factor	X_L/R	X_L/R
6	Amplification	It amplifies voltage	It amplifies current

Numerical:-

Ques Find the impedance current and power factor of the following circuit and draw the phas diagram for? (i) RAL

- (ii) RAC
(iii) R, L, C

in each case the applied voltage is 200 V
frequency is 50 Hz resistance is 10 Ω . Value
of L (circumstance) 50 henry and capacitance ~~100~~
100 μF .

Solution \Rightarrow

$$V = 200 \text{ V}$$

$$R = 10 \Omega$$

$$f = 50 \text{ Hz}$$

$$C = 100 \mu F$$

$$Z = \sqrt{R^2 + (X_L^2 - X_C^2)}$$

$$\begin{aligned} (i) \quad 2\pi fL &= 2 \times \pi \times 50 \times 50 \\ &= 5000\pi \times 10^{-3} \\ &= 15700 \times 10^{-3} \\ &= 15.7 \end{aligned}$$

$$\begin{aligned} Z &= \sqrt{R^2 + (X_L)^2} \\ &= \sqrt{100 + (15.7)^2} \\ &= \sqrt{100 + 246.49} \\ &= \sqrt{346.49} = 18.61 \end{aligned}$$

$$V = ZI$$

$$I = \frac{V}{Z} = \frac{200}{18.61} = 10.74$$



$$\cos \phi = \frac{R}{Z} = \frac{10}{18.61} = 0.54$$

⇒ Three phase (Φ) Balanced circuits :- Star
Delta

⇒ Advantages of 3 phase over 1 phase (Φ) system

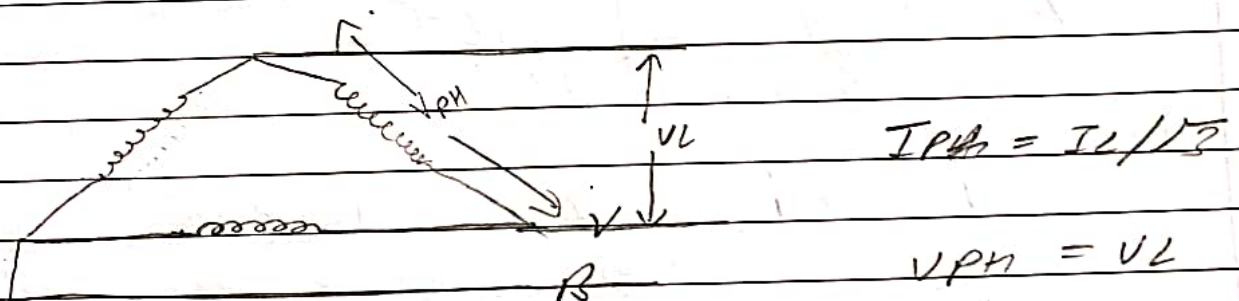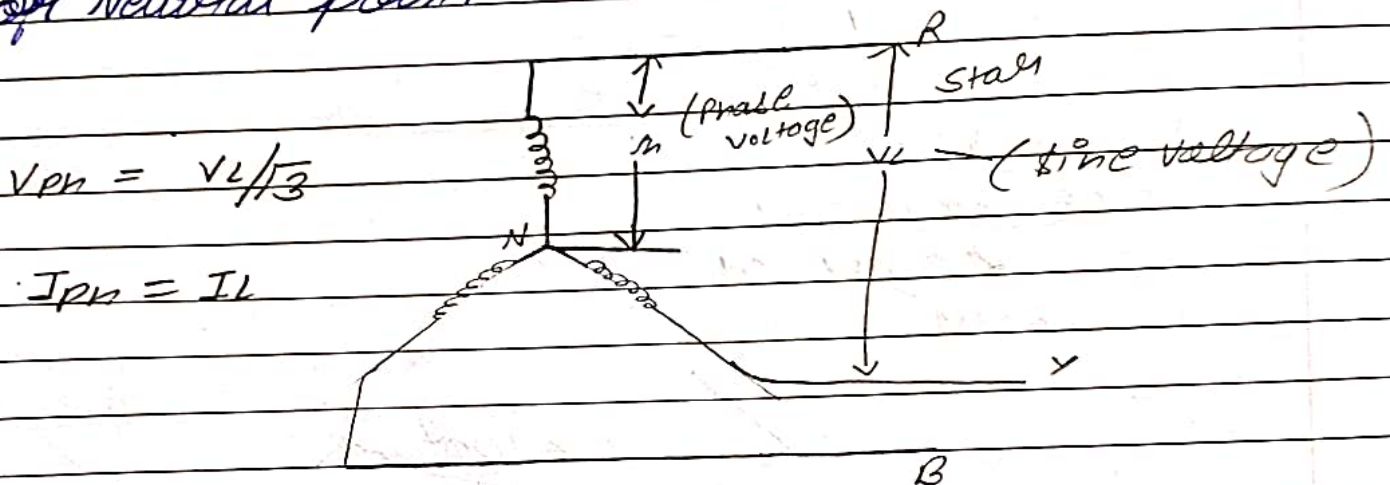- 1) Constant Power
- 2) Higher Rating
- 3) Power Transmission Economical

⇒ In ~~star~~ connection the similar end (either start or finish) of the three winding are connected to a common point called ~~start~~ Neutral point



Unit = III

P.N Junction

Important Energy bands:-

1. > Valance band:- The electrons in the outmost orbit of an atom are known as valance electrons under normal condition of the atom. Valance band contains the e^- of highest energy. This band may be filled completely or partially.
2. > Conduction gap:- In some of the materials for example:- metals the valance e^- are attached to the nucleus and can be reattached very easily. These e^- are known as free e^- and are responsible for the conduction of current.
3. > Forbidden energy gap:- The energy gap b/w the valance band and conduction band is known as forbidden energy gap.

HOL :- A vacancy left in the valance band because of lifting of electron from valance band to conduction band is called HOL.