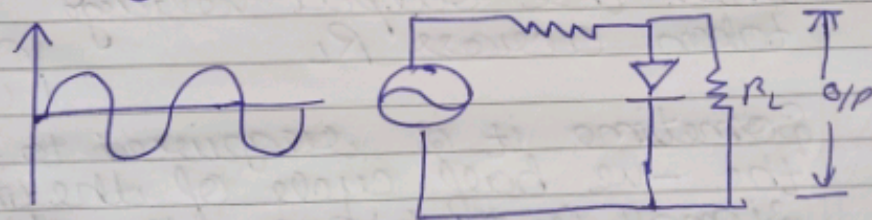



## Clipper:

It is a circuit used to change the shape of an input voltage of an input wave by clipping or removing a portion of it & is called clipping circuit. It is also known as clipper or limiter or slicer. A clipper has the ability to remove signal's voltage above or below a specified level and hence change the wave shape of input signal.

Based on it they are of two types:  
→ ~~Costum~~ Positive Clipper  
→ Negative Clipper.



## Positive Clipper:

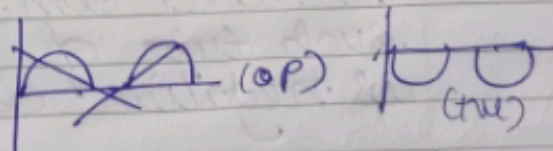

Circuit which removes the half cycle of the signal (input voltage) is called positive clipper.




### Working:

During +ve half cycle of input voltage the diode is forward biased and conducts heavily. Ideally it acts as a closed switch and hence the voltage across the diode or the load is zero due to which +ve half cycle is clipped off.

During negative half cycle the diode is reverse biased and behaves as an open switch. Then the current flows through  $R_L$  and  $R$  which are connected in series in this condition the circuit behaves as a voltage divider while the output voltage is taken across  $R_L$ .

(-ve) (op)

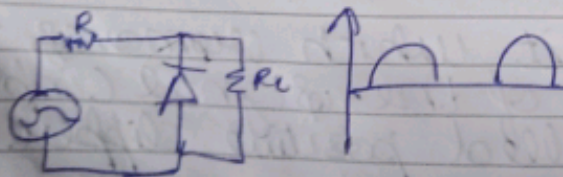Sometimes it is required to remove the -ve half cycle of the input signal. In that case the direction or the polarity of the diode across the load can be easily changed. Such a type of clipper is known as a negative clipper.







## Clamper :

A circuit which shift either positive ~~or~~ or negative peak of the signal at a desired DC level is known as a clamping circuit or clamper.

- Positive Clamper
- Negative Clamper
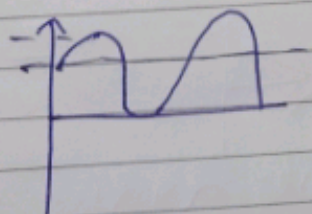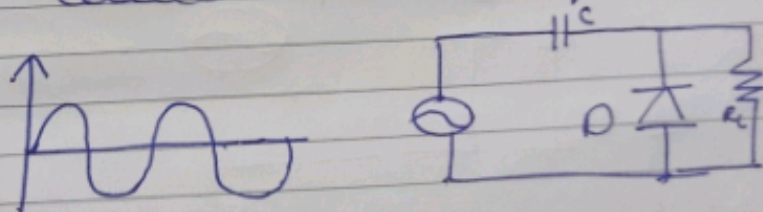
## Positive Clamper :

A circuit which shift the signal in the positive side in such a way that the negative peak of the signal falls on the zero level is called +ve clamper.




It is also known as level shifts / amplification of signal.



# DC Circuits

## Network Analysis / Terms:

Active Element

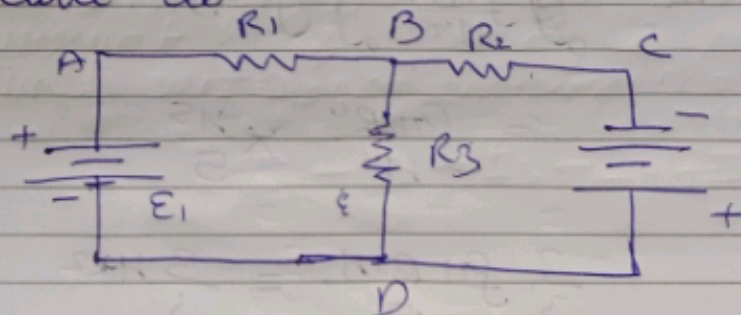

Active Element  $\rightarrow$  The element which supply energy to the circuit is called active element.  $E_1$  &  $E_2$  are active elements.

Passive Element  $\rightarrow$  The element which receives energy is called passive element.  $R_1, R_2, R_3$  (Resistor, inductor and capacitor).

in figure 1  $R_1, R_2$  and  $R_3$  are the passive elements.

Node: It is a point in the network where two or more circuit elements are joint  
A, B, C & D.



\_/\_/\_

Junction: It is a point in the network where 3 or more circuit elements are joined in fact it is a point where current is divided. B & D are the points.

Branch: The part of a network which lies between two junction point is called Branch. A & C.

Loop: The closed path of a network is called loop.  
ABDA & BCD, ABCD

Mesh: The most element any form of a loop which cannot be further divided is called mesh.

Kirchhoff's Law:

Kirchhoff's 1<sup>st</sup> Law / Current law:

This law relates the current flowing through the circuit. Kirchhoff's Current law (KCL) this law states that the algebraic sum of whole the current meeting at a point or junction is zero.